

# Assignment 2

Arnav Yadnopavit  
EE24BTECH11007

April 18, 2025

## 1 Problem 1: Convolution of Two 8-element Vectors

### Objective

Design a Verilog module to perform discrete convolution on two 8-element input vectors (4-bit each).

### Code

1\_convolution.v

```
module convolution(input [31:0] x_in, input [31:0] h_in, output reg
[63:0] y_out);
    integer i,j;
    reg [3:0] x [7:0];
    reg [3:0] h [7:0];
    reg [7:0] temp_y [15:0];
    always @(*) begin
        for (i=0;i<8;i=i+1) begin
            x[i]=x_in[i*4 +: 4];
            h[i]=h_in[i*4 +: 4];
        end
        for (i=0;i<16;i++)
            temp_y[i]=0;
        for (i=0;i<16;i=i+1) begin
            for (j=0;j<8;j=j+1) begin
                if (i>=j&&(i-j)<8) begin
                    temp_y[i]=temp_y[i]+x[i-j]*h[j];
                end
            end
        end
        for (i=0;i<16;i=i+1)
            y_out[i*4 +: 4]=temp_y[i][3:0];
    end
endmodule
```

## 1\_test.v

```
'timescale 1ns/1ps

module test_conv;
reg [31:0] x_in,h_in;
wire [63:0] y_out;

convolution uut(.x_in(x_in),.h_in(h_in),.y_out(y_out));
initial begin
    $dumpfile("conv.vcd");
    $dumpvars(0,test_conv);

    $display("Time\tx_in\tth_in\ty_out");
    $monitor("%0dns\t%b\t%b\t%b", $time, x_in,h_in, y_out);

    x_in = 32'h00000000;h_in = 32'h00000000;#10;
    x_in = 32'hFFFFFFFF;h_in = 32'hFFFFFFFF;#10;
    x_in = 32'h12345678;h_in = 32'h87654321; #10;
    x_in = 32'h10000000;h_in = 32'h12345678; #10;
    x_in = 32'h12345678;h_in = 32'h10000000; #10;
    $finish;
end

endmodule
```

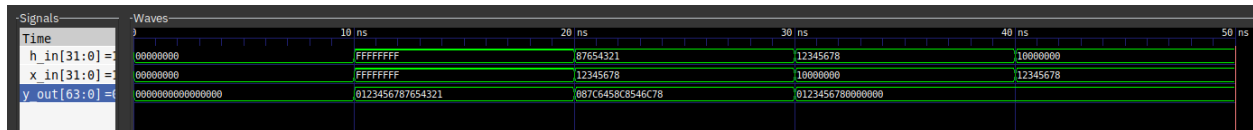


Figure 1: Timing Diagram

## Explanation

This module performs a discrete convolution using nested loops over two 8-element arrays. For each output index, it computes the sum of products of overlapping elements. Overflow is ignored by truncating the result to 4 bits.

## 2 Problem 2: 8-bit Full Adder Using Loop

### Objective

Design an 8-bit full adder using generate block (loop statement).

## Code

### 2\_adder.v

```
module EightBitAdder(input [7:0] a,input [7:0] b,output [7:0] sum,
    output cout);
    genvar i;
    wire [8:0] c;
    assign c[0]=0;
    generate
        for(i=0;i<8;i=i+1) begin
            bitadder adders(.a(a[i]),.b(b[i]),.sum(sum[i]),.cin(
                c[i]),.cout(c[i+1]));
        end
    endgenerate
    assign cout=c[8];
endmodule

module bitadder(input a,input b,input cin, output sum,output cout);
    assign sum=a^b^cin;
    assign cout=a&b|b&cin|cin&a;
endmodule
```

### 2\_test.v

```
`timescale 1ns/1ps

module test_8bitadder;

    reg [7:0] a,b;
    wire [7:0] sum;
    wire cout;

    EightBitAdder dusra(.a(a),.b(b),.sum(sum),.cout(cout));

    initial begin
        $dumpfile("8bitadder.vcd");
        $dumpvars(0,test_8bitadder);

        $display("Time\ta\tb\tsum\tcout");
        $monitor("%0dns\t%b\t%b\t%b\t%b", $time, a,b, sum,cout);
        a=8'b00000000;b=8'b00000000;#10;
        a=8'b11111111;b=8'b11111111;#10;
        a=8'b10101010;b=8'b11111111;#10;
        a=8'b10111011;b=8'b10101110;#10;
        a=8'b11010101;b=8'b10011101;#10;

        $finish;
    end
end
```

```
endmodule
```

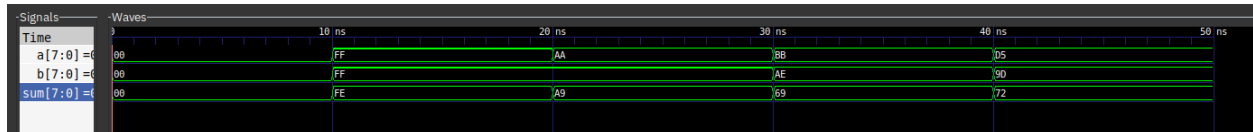


Figure 2: Timing Diagram

## Explanation

The adder uses a generate block to instantiate 8 full adders for each bit. Carry propagates through a wire array. No arithmetic operators are used.

## 3 Problem 3: 4-bit Ripple Carry Adder using NAND Gates

### Objective

Create a 4-bit ripple carry adder using only 2-input NAND gates with 1 ns delay.

### Code

#### 3\_nandcounter.v

```
'timescale 1ns/1ps
module RippleAdder(input [3:0]a,input [3:0]b,output [3:0] sum,output
    cout);
    genvar i;
    wire [4:0] c;
    assign c[0]=0;
    generate
        for(i=0;i<4;i=i+1)begin
            bitadder adders(.a(a[i]),.b(b[i]),.sum(sum[i]),.cin(
                c[i]),.cout(c[i+1]));
        end
    endgenerate
    assign cout=c[4];
endmodule
module bitadder(input a,input b,input cin,output cout, output sum);
    wire ws1;
    xorgate w1(ws1,a,b);
    xorgate w2(sum,cin,ws1);
    wire wc1,wc2,wc3,wc4;
    andgate ww1(wc1,a,b);
    andgate ww2(wc2,b,cin);
```

```

andgate w3(wc3,cin,a);
orgate w4(wc4,wc1,wc2);
orgate w5(cout,wc4,wc3);

endmodule
module xorgate(output o,input a, input b);
wire w1,w2,w3;
nandgate ww1(w1,a,b);
nandgate ww2(w2,a,w1);
nandgate ww3(w3,b,w1);
nandgate ww4(o,w2,w3);
endmodule
module andgate(output o,input a,input b);
wire w1,w2;
nandgate ww1(w1,a,b);
nandgate ww2(w2,a,b);
nandgate ww3(o,w1,w2);
endmodule
module orgate(output o,input a,input b);
wire w1,w2;
nandgate ww1(w1,a,a);
nandgate ww2(w2,b,b);
nandgate ww3(o,w1,w2);
endmodule
module nandgate(output o,input a,input b);
assign #1 o=~(a&b);
endmodule

```

### 3\_test.v

```

`timescale 1ns/1ps

module test_RippleAdder;

reg [3:0]a,b;
wire [3:0] sum;
wire cout;

RippleAdder tistra(.a(a),.b(b),.sum(sum),.cout(cout));

initial begin
    $dumpfile("8bitadder.vcd");
    $dumpvars(0,tistra);

    $display("Time\ta\tb\tsum\tcout");
    $monitor("%0dns\t%b\t%b\t%b\t%b", $time, a,b, sum,cout);
    a=4'b0000;b=4'b0000;#20;
    a=4'b1111;b=4'b1111;#20;

```

```

        a=4'b1010;b=4'b1111;#20;
        a=4'b1011;b=4'b1110;#20;
        a=4'b0101;b=4'b1101;#20;

        $finish;
end
endmodule

```

 


Figure 3: Timing Diagram

## Explanation

The 4-bit ripple carry adder is implemented entirely using 2-input NAND gates. XOR, AND, and OR gates are constructed from NANDs. Delay per gate is set to 1 ns, and the ripple-carry effect propagates through the bitadder stages. Each bit's carry is passed to the next stage, emulating the behavior of a ripple-carry adder structurally.

## Propagation Delay Analysis

### Gate Delay Assumptions

Each 2-input NAND gate has a delay of 1 ns. All logic gates are built from these NANDs:

$$\text{XOR (4 NANDs)} \Rightarrow 4 \times 1 \text{ ns} = 4 \text{ ns},$$

$$\text{AND (3 NANDs)} \Rightarrow 3 \times 1 \text{ ns} = 3 \text{ ns},$$

$$\text{OR (3 NANDs)} \Rightarrow 3 \times 1 \text{ ns} = 3 \text{ ns}.$$

### Full Adder (bitadder) Delay

Each 1-bit full adder has two paths:

$$\text{Sum path: } 2 \text{ XORs} = 4 \text{ ns} + 4 \text{ ns} = 8 \text{ ns},$$

$$\text{Carry path: } 3 \text{ ANDs} + 2 \text{ ORs} = 3 \times 3 \text{ ns} + 2 \times 3 \text{ ns} = 9 \text{ ns} + 6 \text{ ns} = 15 \text{ ns}.$$


### Worst-Case Delay for 4-bit Ripple Carry Adder

The carry ripples through three full-adder stages before the final sum bit:


$$\text{Total worst-case delay} = 4 \times (\text{carry delay}) + (\text{sum delay}) = 4 \times 15 \text{ ns} + 4 \times 8 \text{ ns} = \boxed{82 \text{ ns}}.$$

## Module Gatelevel Diagrams


### 3.1 XOR

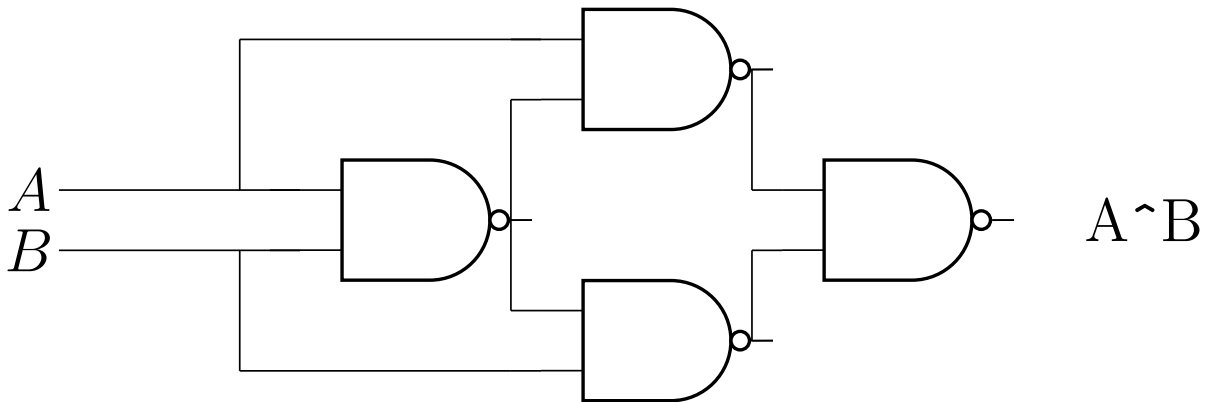



### 3.2 AND

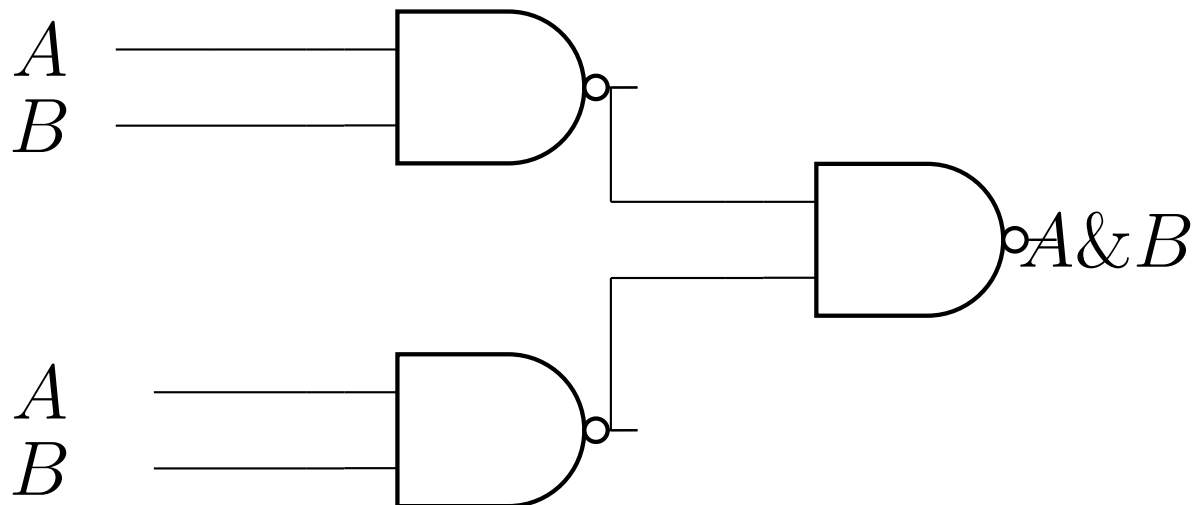

### 3.3 OR

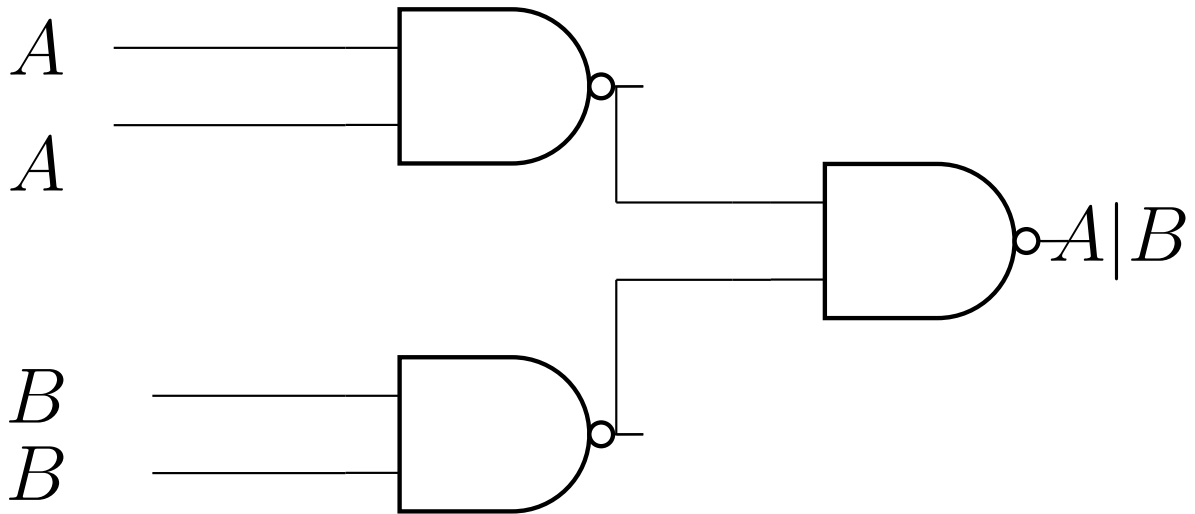

### 3.4 Full Adder

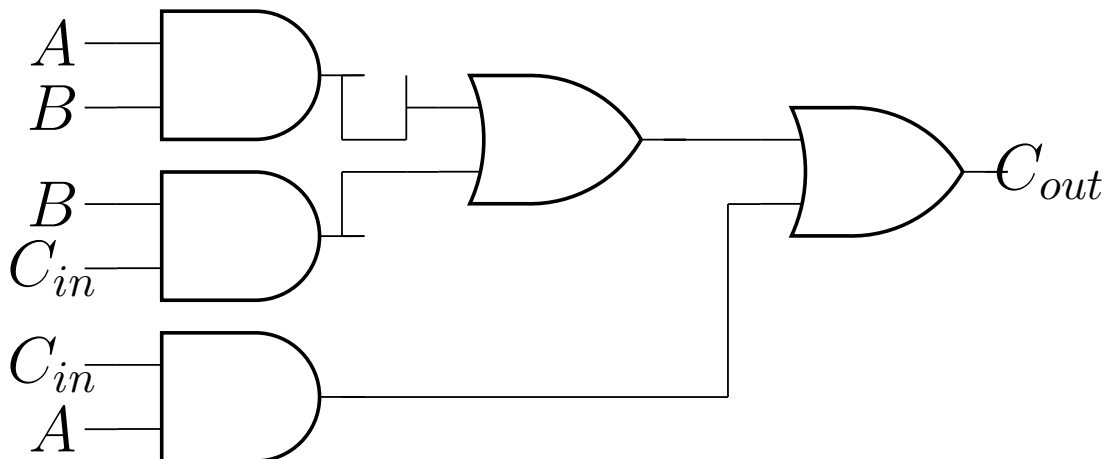 

For codes,figs etc refer to

□



Thank You